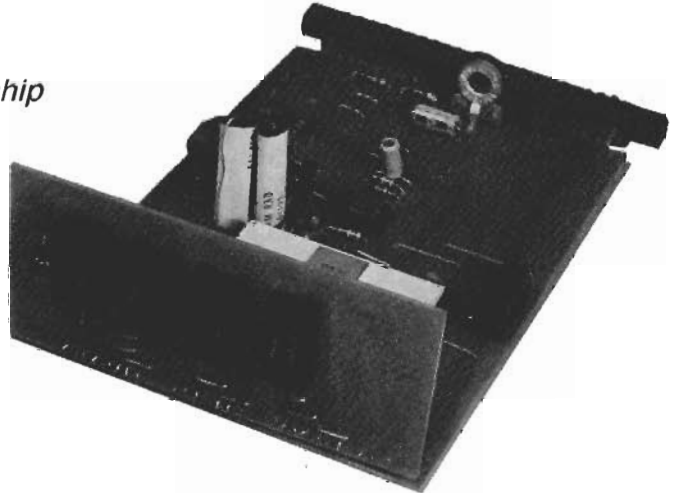


# BUILD

## 3½-Digit DMM

*The digital panel meter has the same relationship to the DMM as the D'Arsonval panel meter has to the analog multimeter. Build your own multimeter using a DPM*

**DR. E. H. BORNEMAN AND ROBERT BENWARD**




A DIGITAL PANEL METER IS THE HEART OF every digital multimeter. This article describes a relatively simple circuit for a 2-volt DPM (*Digital Panel Meter*) using readily available IC's that can be easily converted into a digital multimeter (DMM) by adding some voltage-divider and current-shunting circuits. The resulting instrument, including power supply, can be simply packaged to become a very functional and rather attractive digital multimeter.
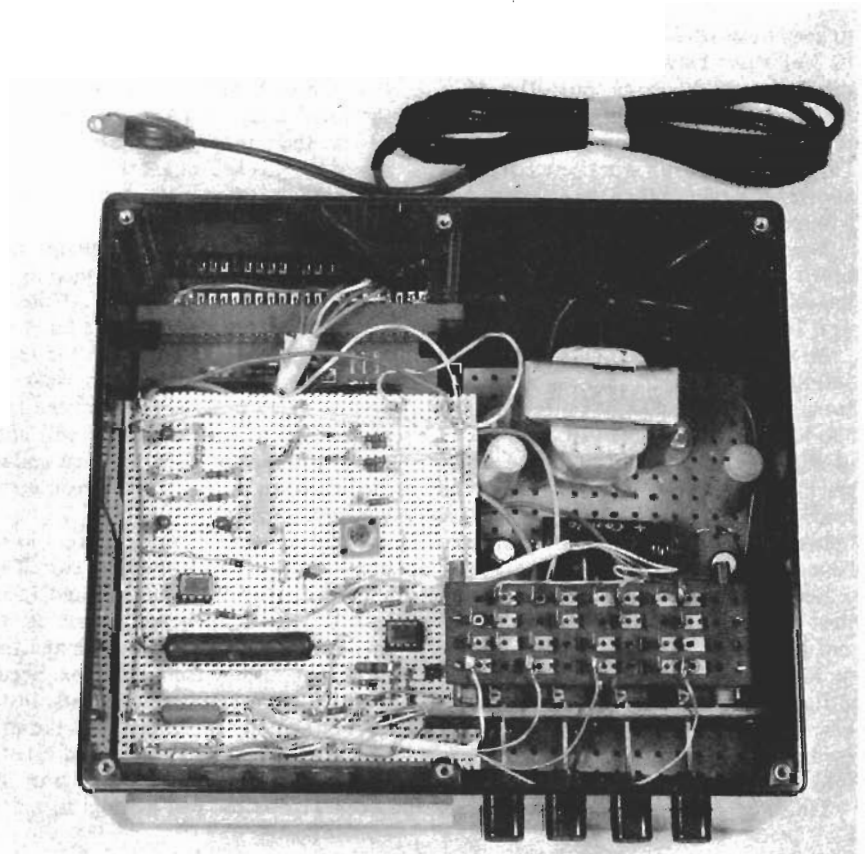
### DPM circuit and operation

The basic DPM circuit is shown in Fig. 1. It uses a minimum number of parts, with most of the circuitry in two IC's; one a signal conditioner, the other a digital processor. These IC's include an on-board clock and a medium quality internal reference (40 ppm/°C). The measuring system uses dual-slope integration with its advantages of noncritical clock frequency, high rejection of AC signals and use of noncritical components.

The 8052 signal conditioner has three phases of signal conversion, these being auto-zero, integrate input and integrate reference. At the end of a measurement the system automatically reverts to auto-zero mode until a new measurement is started. If no overload has occurred in the previous measurement, it takes 10 milliseconds for the auto-zero to null. At power-on or after an overload it takes 100



**INTERIOR OF A DIGITAL MULTIMETER** based on a version of the digital panel meter in the head photo above. The DPM (at left) used point-to-point wiring on perforated board. See Fig. 8 for layout drawing.

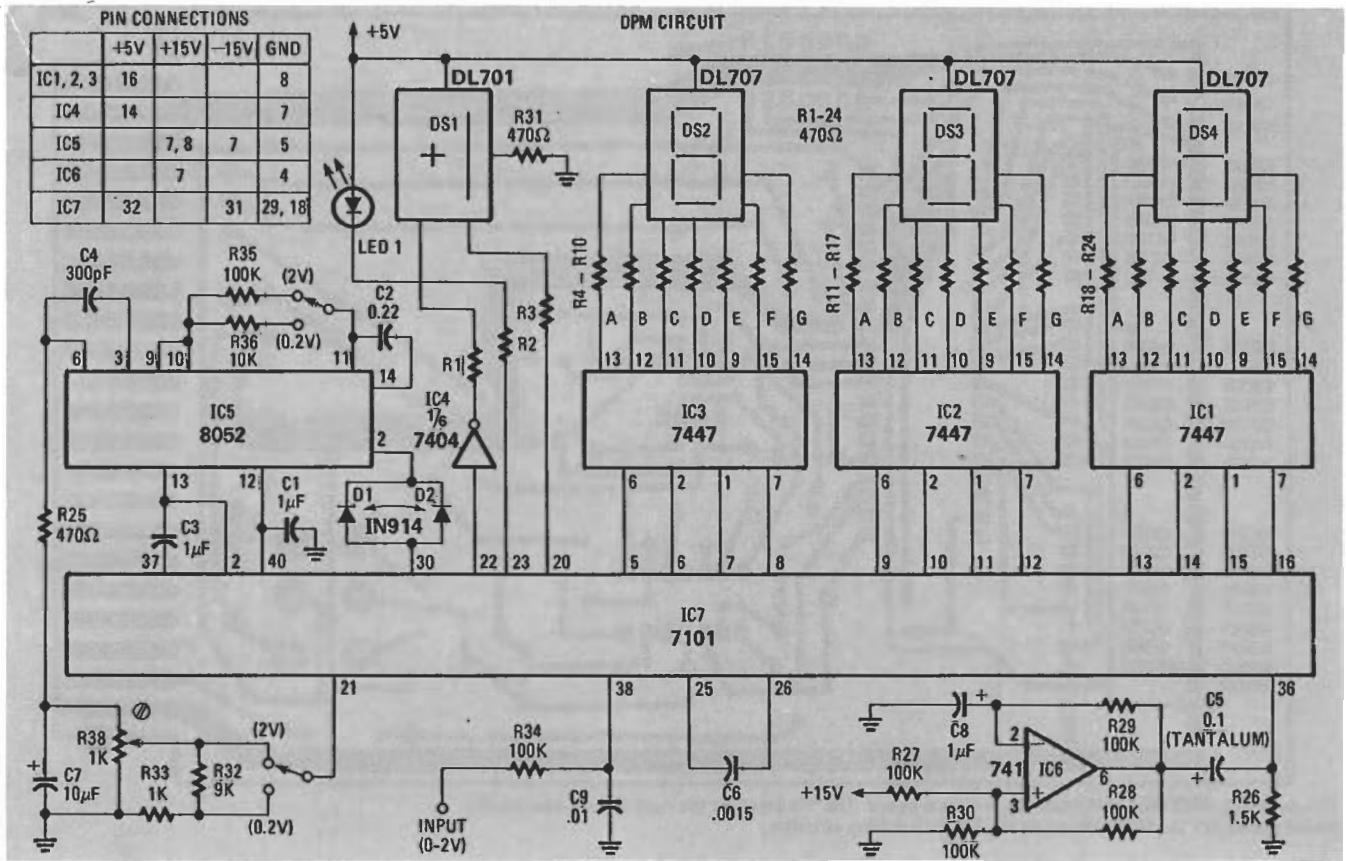


FIG. 1—DIGITAL PANEL METER SCHEMATIC. The unit is simple and easy to construct; using either point-to-point wiring or a couple of PC boards.

### DPM PARTS LIST

All resistors 1/4 watt, 10% or better

R1, R2, R4-R25, R31—470 ohms  
 R26—1500 ohms  
 R27-R30, R34, R35—100,000 ohms  
 R32—9000 ohms  
 R33—1000 ohms  
 R36—10,000 ohms  
 R38—1000 ohms, miniature potentiometer

All capacitors 10 volts DC or higher

C1, C3—1  $\mu$ F, Mylar

C2—0.22  $\mu$ F, polypropylene

C4—300 pF, disc  
 C5—0.1  $\mu$ F, tantalum or metallized film  
 C6—.0015  $\mu$ F, disc  
 C7—10  $\mu$ F, electrolytic  
 C8—1  $\mu$ F, electrolytic  
 C9—0.01  $\mu$ F, disc

#### Semiconductors

D1, D2—1N914 diode  
 DS1—+1 LED digit, Litronix DL701 or equal

DIS2-DIS4—7-segment LED digit, Litronix DL707 or equal

LED1—Red LED, 0.2-in. diameter

#### Integrated circuits

IC1-IC3—7447 BCD/7-segment decoder/driver  
 IC4—7404 hex inverter  
 IC5—8052 signal conditioner  
 IC6—741 op-amp  
 IC7—7101 digital processor

milliseconds to null.

None of the circuit component values are critical in determining the accuracy of the instrument. For example, the reference capacitor and auto-zero capacitor (C1 and C3) are both shown as 1.0  $\mu$ F. These rather large values minimize the effect of PC board leakage. The 0.22- $\mu$ F value of the integration capacitor C2 is selected for PC board considerations alone, since the very small leakage at the integration input is nulled at auto-zero. It

is very important that this capacitor have very low dielectric absorption.

The DPM is calibrated by putting a standard mercury cell across the input (any convenient reference source less than 2 volts can be used) and adjusting the 1K pot until the reference voltage is correctly displayed on the readout.

Initially the DPM circuit was built on a perf board, but the later models were constructed on two PC boards with one board containing the displays and the second, with a 15-pin edge connector, containing all the circuitry.

The foil pattern for the main PC board is in Fig. 2. The parts are positioned as shown in Fig. 3. Figure 4 is the pattern for the display board. Figure 5-a shows the jumpers that are installed from the front side of the board. Figure 5-b shows the locations of three jumpers connected to the 7-segment displays. The drawings in Fig. 5-c show how the jumpers can be added. The main and display boards are

joined by 26 jumpers as detailed in Fig. 3 and Fig. 5-d.

Start with scraps of leads clipped off the resistors and other components that have been installed. Insert the leads from the foil side of the display board and solder in place. Insert the unattached lead ends in the holes in the main board, adjust the boards so they are close together and at right angles. Solder one end, check board alignment and then solder the other. Solder the connections between the ends.

Electrical characteristics of the DPM are as follows:

**Power supply:** +5 V @ 200 mA;  
 +15 V @ 25 mA; -15 V @ 25 mA.

**Linearity (full scale):** 0.1 count typ.;  
 +1 count max.

**Rollover [differential in equal (+V = -V = 2V)]:** 0.1 count typ.;  
 +1 count max.

**Noise (full scale):** -0.05 counts  
**Leakage current into input:** 5 pA typ.;  
 30 pA max.

The following are available from Hobbi House, 969 Ball Ave., Union, NJ 07083 (800-631-7485).

Digital Panel Meter, includes all parts listed in the DPM Parts List plus PC boards, \$29.95.

Set of PC boards for DPM (2 boards), \$6.95.

Digital Multimeter, includes all parts listed in DMM, DPM and Power Supply Parts Lists, \$49.95.

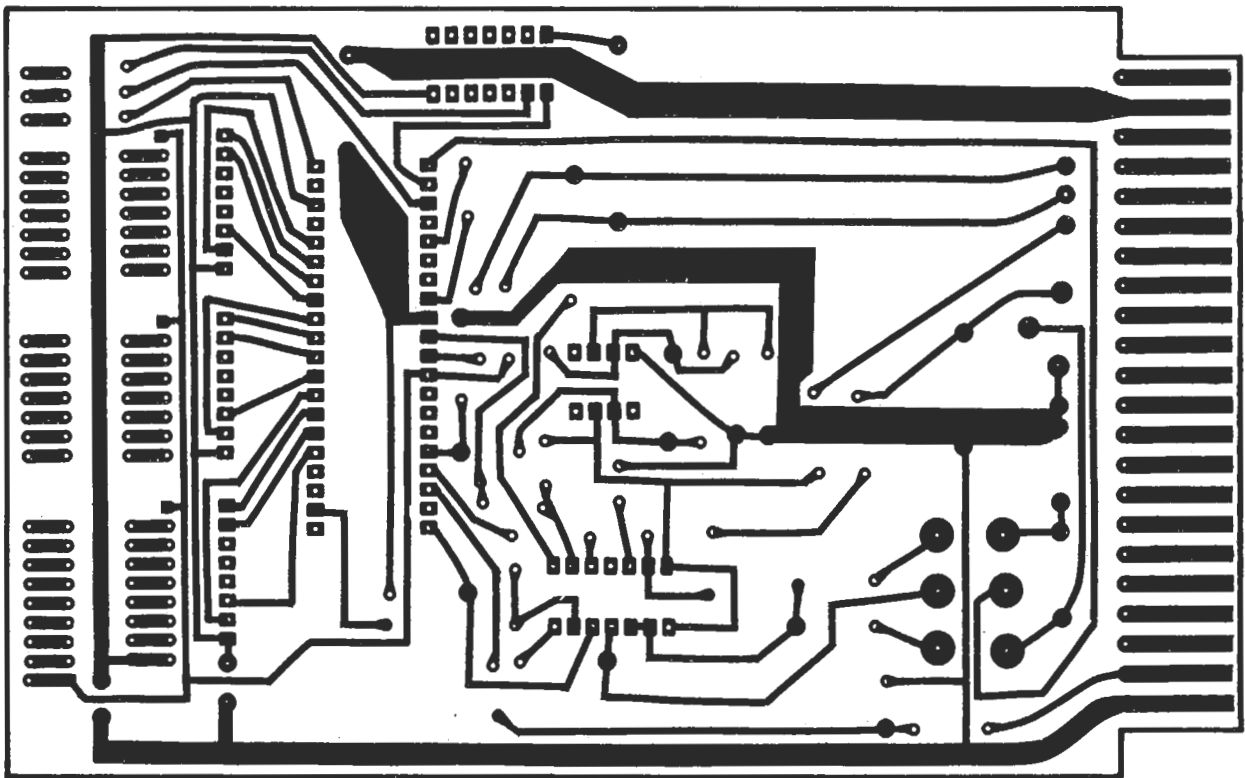


FIG. 2—FULL-SIZE FOIL PATTERN for the main board. The "fingers" on the right fit into a female PC board connector for connections to the DMM switching circuitry.

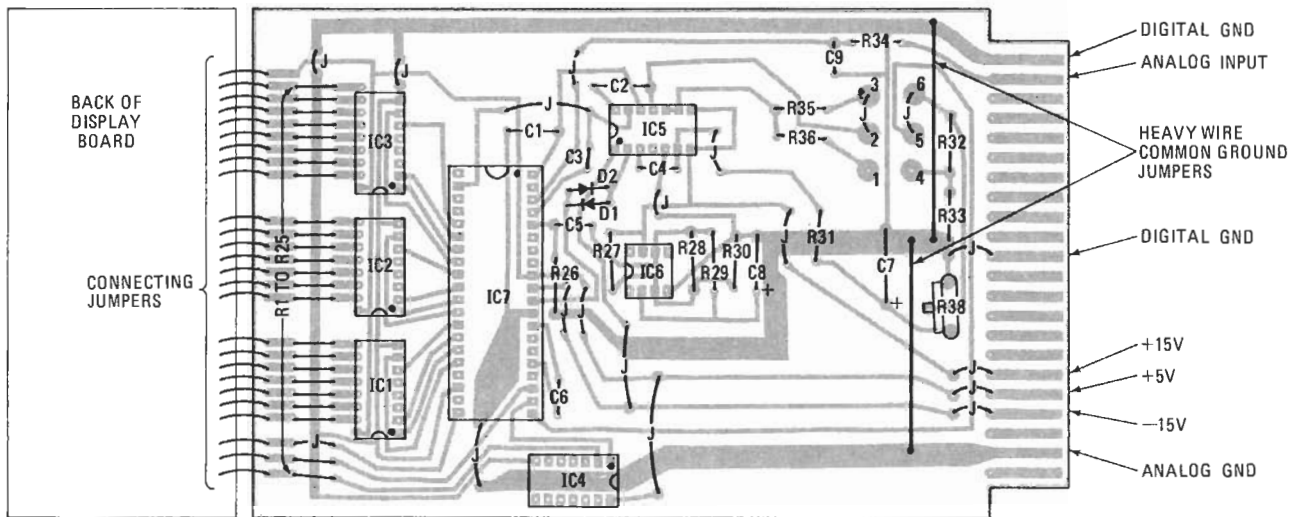


FIG. 3—HOW COMPONENTS ARE PLACED on the main board. Note the location of jumpers, IC positioning and electrolytic capacitor lead polarity.

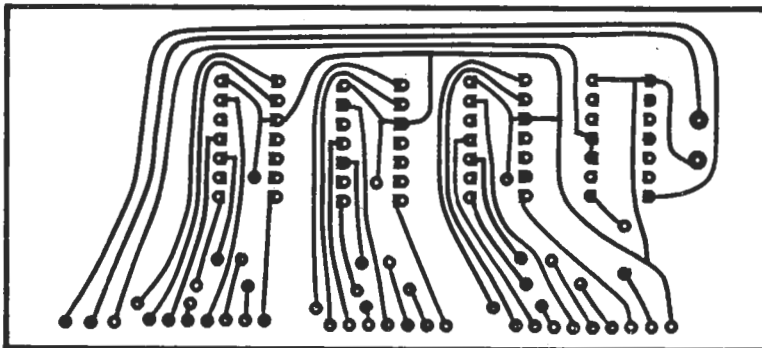



FIG. 4—DISPLAY BOARD foil pattern is full-size. Jumpers must be installed on both sides of the board as detailed in another figure.

The power supply for the DPM must deliver regulated outputs of +5 volts, +15 volts, and -15 volts DC. A circuit diagram for the power supply is shown in Fig. 6.


Although rather low currents are required for the DPM, the output currents supplied by this circuit will operate all the additional functions of the multimeter circuitry to be described. Good regulation is required (0.1%), so three voltage regulator IC's are used.

#### Conversion of DPM into digital multimeter

The basic DPM can be converted into a

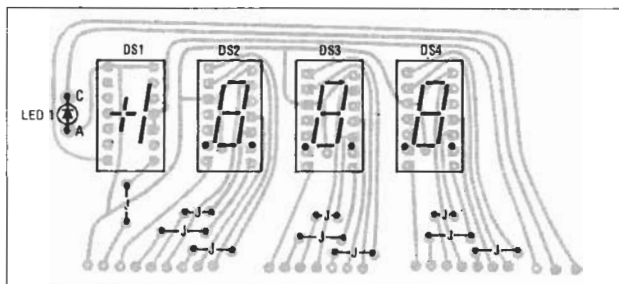

a DISPLAY BOARD FRONT

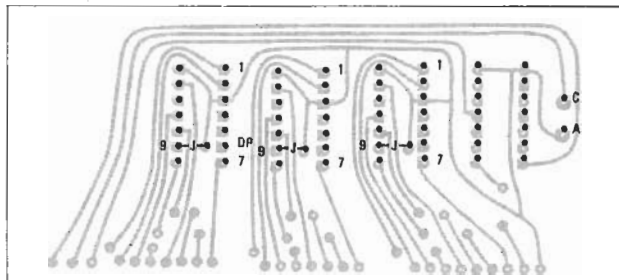

b DISPLAY BOARD BACK


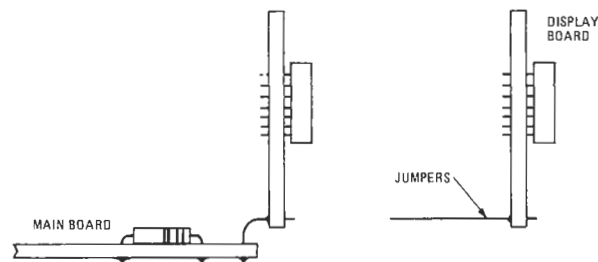
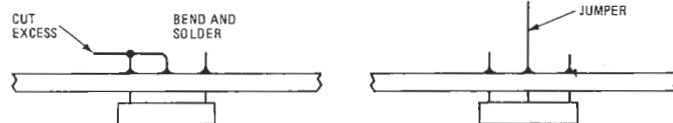


FIG. 5—MOUNTING AND JUMPER DETAILS for display board. Drawing c shows how back-of-board jumpers are formed while d, along with Fig. 3 shows how boards are joined by jumpers.

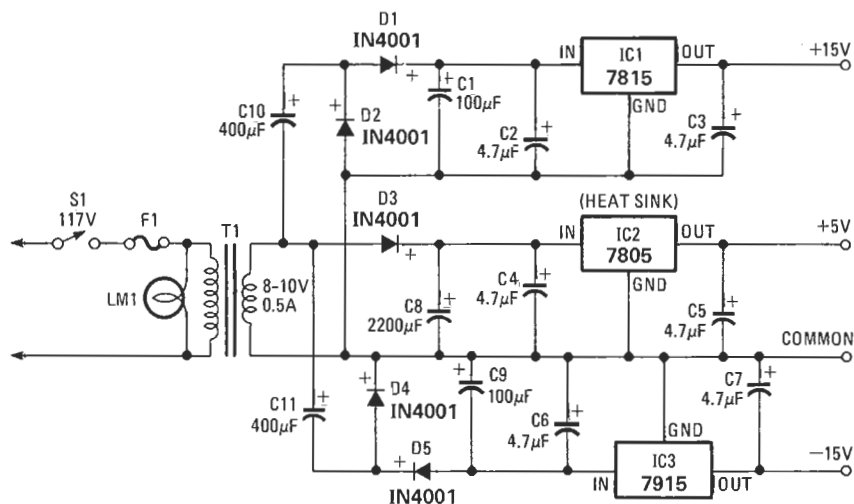

### POWER SUPPLY PARTS LIST

#### Capacitors 25 volts DC or higher

- C1, C9—100  $\mu$ F, electrolytic
- C2—C7—4.7  $\mu$ F, tantalum
- C8—2200  $\mu$ F, electrolytic
- C10, C11—400  $\mu$ F, electrolytic

#### Semiconductors

- D1—D5—1N4001 diodes
- IC1—7815 positive 15-volt regulator
- IC2—7805 positive 5-volt regulator
- IC3—7915 negative 15-volt regulator
- S1—SPST switch
- T1—power transformer, 8-10-volt, 0.5-A secondary
- LM1—117-volt pilot lamp
- F1—0.25-ampere fuse

FIG. 6—POWER SUPPLY DIAGRAM. Three solid-state voltage regulators set the levels of voltages needed to operate the multimeter.

digital multimeter by adding the circuitry shown in Fig. 7. This circuit uses push-button DPDT switches. However, these can be replaced with a multisection rotary switch. Functions performed by the digital multimeter are listed in the following table.

**DC volts:** 2, 20, 200, 2000

- AC volts:** 2, 20, 200, 2000 (RMS)
- Ohms:** 2K, 20K, 200K, 2 megohms, 20 megohms
- Direct current:** 200 mA, 2A, 10A
- Alternating current:** 200 mA, 2A, 10A (RMS)

The circuit shown in Fig. 7 connects directly into the input of the 2-volt DPM.

Accuracy of the multimeter functions depends on the precision resistors used in the voltage-divider and current-shunt circuits. I recommend 1% or better, to take advantage of the inherent high accuracy of the DPM. Unless otherwise indicated, all other resistors in the circuit are  $\frac{1}{4}$  watt, 10%.

#### All resistors $\frac{1}{4}$ watt, 5% unless noted


- R1—9 megohms,  $\frac{1}{2}$  watt, 1% or better
- R2—900,000 ohms,  $\frac{1}{4}$  watt, 1% or better
- R3—90,000 ohms,  $\frac{1}{4}$  watt, 1% or better
- R4—9000 ohms,  $\frac{1}{4}$  watt, 1% or better
- R5—1000 ohms,  $\frac{1}{4}$  watt, 1% or better
- R6—0.1 ohm, 10 watts (20 watts optional) 1% or better
- R7—1.0 ohm, 10 watts, 1% or better
- R8—10 ohms, 1 watt, 1% or better
- R9—100 ohms,  $\frac{1}{2}$  watt
- R10, R30—30,000 ohms
- R11, R21—1 megohm
- R12—10 megohms

#### ADD-ON MULTIMETER PARTS

- R13—6200 ohms
- R14—750 ohms
- R15—4300 ohms
- R16—910 ohms
- R17—1000 ohms, miniature potentiometer
- R18—4700 ohms
- R19, R23—3300 ohms
- R20, R22—9100 ohms
- R24—470,000 ohms
- R25, R26—10,000 ohms
- R27, R29—5100 ohms
- R28—2500 ohms, miniature potentiometer
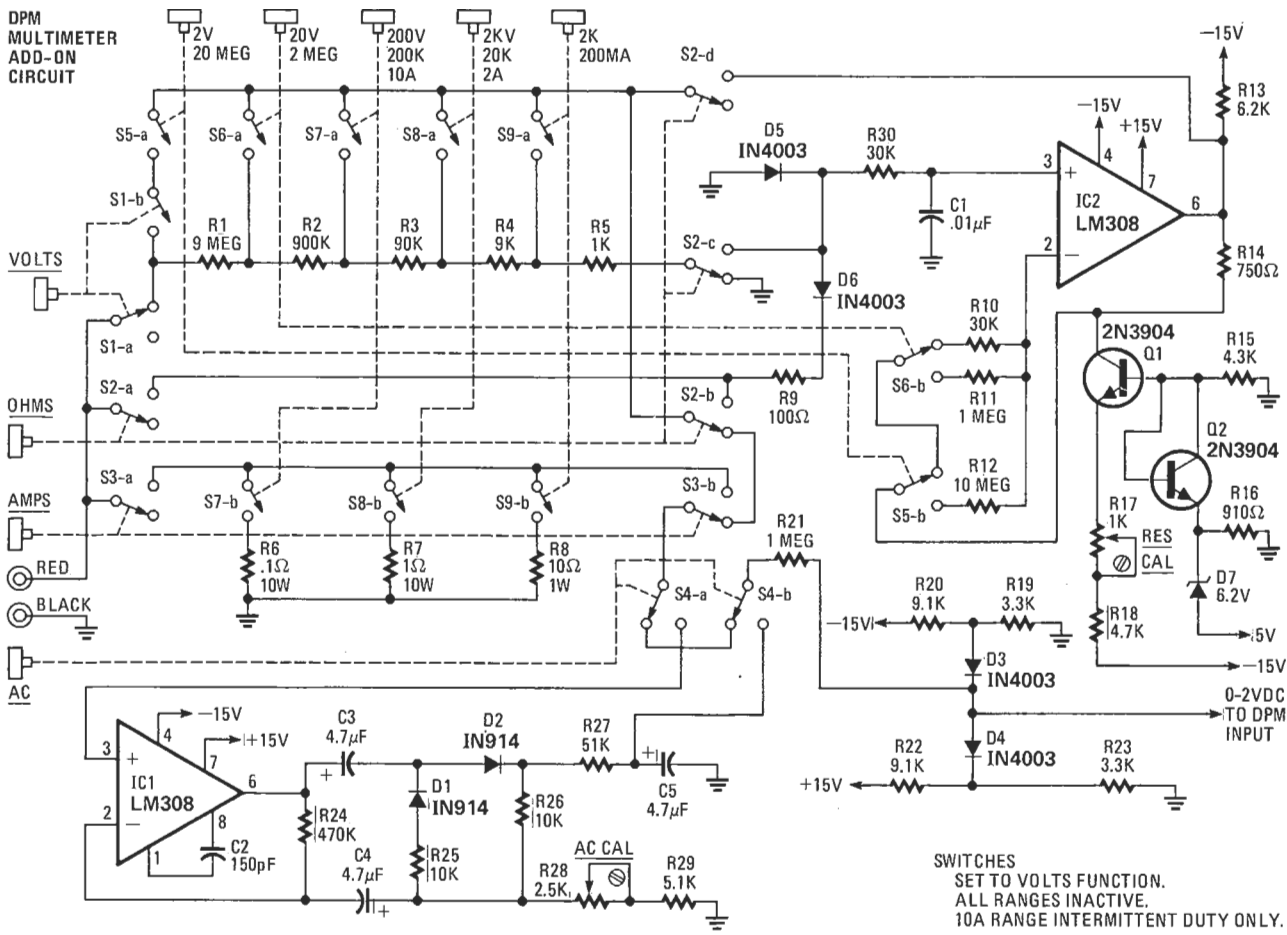
#### All capacitors 25-volts DC or higher

- C1—.01  $\mu$ F, ceramic
  - C2—150 pF, ceramic
  - C3—C5—4.7  $\mu$ F, tantalum
- #### Semiconductors
- D1, D2—1N914
  - D3—D6—1N4003
  - D7—6.2-volt Zener diode
  - Q1, Q2—2N3904
  - IC1, IC2—LM308 op-amps
- #### Miscellaneous
- S1, S3—S9—DPDT pushbutton switch or equivalent
  - S2—4-pole DT pushbutton switch or equivalent



SWITCHES  
SET TO VOLTS FUNCTION.  
ALL RANGES INACTIVE.  
10A RANGE INTERMITTENT DUTY ONLY.

FIG. 7—CIRCUITRY TO CONVERT DPM TO DMM includes function selector switching, multiplier and shunt resistor networks and a few active components.

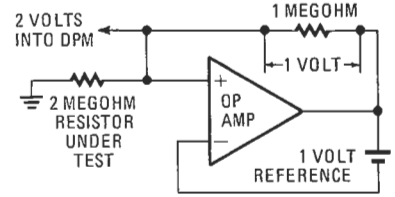
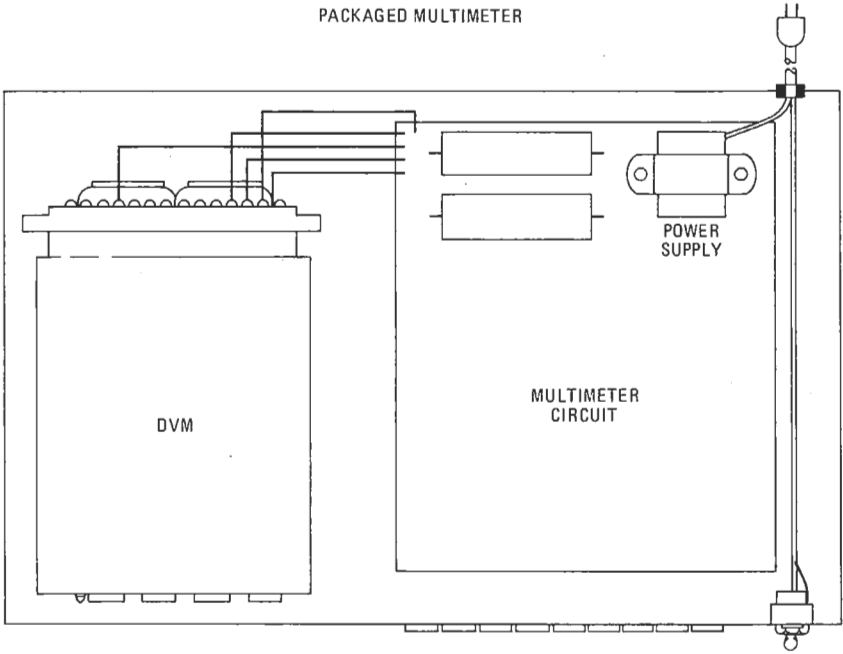


FIG. 9—SIMPLIFIED OHMMETER CIRCUIT. Equal voltages at op-amp inputs are essential to proper ohmmeter operation.

The multimeter can now be made into a finished packaged instrument by housing it in a chassis case similar to that shown in Fig. 8 and the photograph. Here the basic DPM is mounted on the left side of the chassis with the display showing through a tinted red or gray acrylic plastic window, the power supply plus multimeter circuitry being housed in the right side. On-off and function switches are mounted in the right front panel. Such a packaged instrument, though home built, can offer a very attractive and useful meter for both amateur and professional use.

**DMM operation**

The DMM circuit is built around relatively simple and well-proven circuit principles. The circuit diagram in Fig. 7 shows all functions are fed into the DPM on the 0-2VDC scale. The DC voltage input to the DMM feeds into a precision resistor voltage divider, with the scale

*continued on page 103*

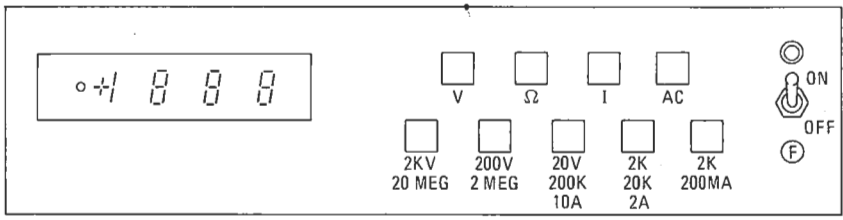


FIG. 8—HOW BASIC PARTS ARE LAID OUT in a typical instrument case. The DPM connects to the multimeter circuit through an edge connector and a short length of cable.

### 3½ DIGIT DMM

*continued from page 44*

---

switches arranged so that the maximum coming off the divider into the DPM input is always 2 volts.

The AC volts input goes through the same voltage divider and then into a "precision rectifier circuit" that converts the signal into DC to feed the input to the DPM. The 2.5K pot in this circuit lets you calibrate the output of the precision rectifier on a one-time basis against a standard AC input signal.

The ohmmeter circuit is shown in simplified form in Fig. 9. Here, one leg of the op-amp contains a standard reference voltage that is adjustable through the 1K pot to exactly 1 volt. The other leg contains the portion of the voltage divider that is active for measuring a particular resistance range. In the illustration the 1-meg resistor shown is used to measure 2 megohms full scale. Since the op-amp operation dictates that the inputs to both legs must be equal, and since the outputs are common, exactly 1 volt must also appear across the 1-meg resistance. This constant voltage forces a constant current through the resistance being measured; in this particular case 2 megohms. The 2 volts developed across the 2-megohm resistor is then fed into the DPM, registering a full-scale reading. Other resistance values for the unknown will, of course, produce proportional voltages feeding into the DPM.

The resistance circuit is calibrated on a one-time basis by adjusting the 1K pot with a standard resistor across the input. When the DPM registers the correct reading of resistance, it has been calibrated. An alternate method is to adjust the pot so that exactly 1 volt appears across the 750-ohm resistor (R14) at the output of the op-amp.

The direct current input is taken off the three shunt resistors, R6, R7 and R8. Each resistor develops exactly 2 volts across it for maximum scale readings. Note that the high current scale is limited to 10 amps only because of the low wattage (10 watts) of the 0.1-ohm resistor (R6). If you make this a 20-watt resistor, you can read 20 A full scale. These resistors should be at least 1 percent tolerance or better for good measurement accuracy.

The multicontact pushbutton switches shown in the circuit diagram are of course the easiest to wire, although layered rotary switches can also be used. The correct decimal point for each scale can be displayed by connecting pin 6 of the appropriate display number (DS-2, 3 or 4) through the appropriate scale switch to ground through a 470-ohm resistor.

The entire DMM circuit can easily be laid out and assembled on a 4½ × 6-inch piece of perforated circuit board with 0.1-inch hole spacings. **R-E**