

Above: View inside the prototype. The unit can be powered from either a battery, a plugback supply, or a source within the frequency meter itself.

We recommend the use of PC stakes or pins for connections to the PCB.

Various options are open to the constructor as far as the sockets and power supply is concerned. We used RCA sockets, but BNC sockets could be used if these suit your frequency meter. The prescaler can be powered from either a suitable source within the frequency meter itself, a small 9V battery within the utility box, or from a plugback supply, as mentioned above.

If battery operation is envisaged, a switch will have to be provided and mounted where we have placed the

PARTS LIST

- 1 PCB, 80f3, 57 x 83mm
- 1 plastic utility box 130 x 68 x 41mm or similar
- 1 Scotchcal front panel 125 x 62mm
- 2 RCA sockets
- 1 2.1mm DC input socket to suit plugpack
- 1 CA3140 op amp
- 1 4011 quad two-input NAND gate
- 2 4017 decade counters
- 1 4046 phase-locked loop

RESISTORS


- ($\frac{1}{4}$ or $\frac{1}{2}$ W, 10% tolerance)
- 3 x 1M, 1 x 330k, 1 x 100k, 2 x 10k, 1 x 1k, 1 x 330 ohms.

CAPACITORS

- 1 x .01uF metallised polyester
- 1 x 0.1uF metallised polyester
- 1 x 1.5uF/15VW tantalum electrolytic
- 1 x 15uF/15VW tantalum electrolytic

Miscellaneous: screws, nuts, scrap aluminium, hook up wire, shielded cable, etc.

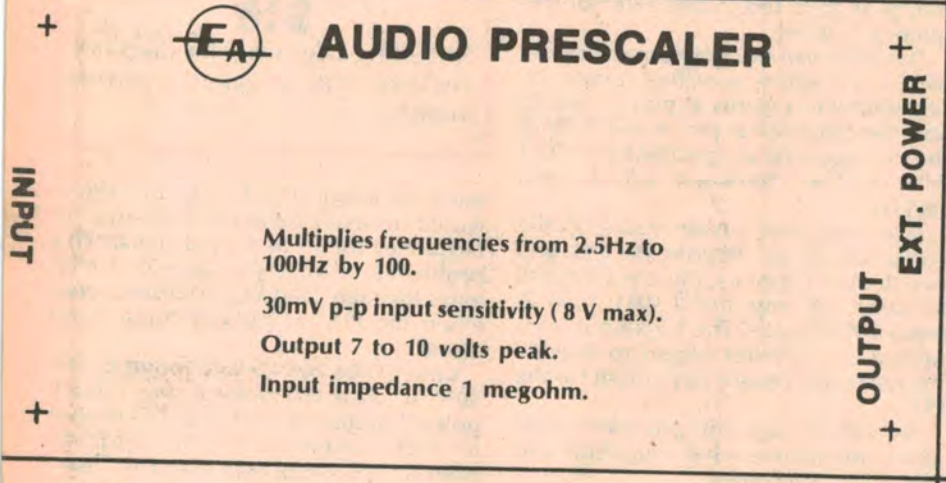Note: Capacitors and resistors with higher ratings may be used if physically compatible. Other substitutions, unless mentioned in the text, are not recommended.



Here is an actual-size reproduction of the front panel artwork.

on the external frequency counter.

When IC2d gates the free-running VCO output off, its output is high, ie, approximately 7V DC. For this reason, IC2d is fed to IC2c to invert the output and results in a "quiescent" level of zero volts DC when no signal is present. The remaining gate in the 4011 package is unused.

The range over which the VCO will oscillate is supply voltage dependent and hence the zener diode incorporated within IC3 is used for voltage stabilisation. With the circuit as shown an input voltage variation of 7 to 15V can be coped with. Current drain is about 10 milliamps. The unit can be powered from a nine-volt battery or a mains plugpack supply.

CONSTRUCTION

Our version was made up in a plastic utility box measuring 130 x 68 x 41mm.

A Scotchcal panel for the lid provides an attractive finish to the prescaler. Alternatively, there may be sufficient room within your frequency meter to accommodate the prescaler.

The circuitry is accommodated on a small PC board measuring 57 x 83mm (coded 80f3) which is mounted to the base of the utility box with two screws.

Start assembly of the PCB with the capacitors and resistors, leaving the CMOS IC's till last. Take the usual precautions when soldering CMOS devices. Connect the soldering iron barrel to the negative supply pattern on the PCB, using a clip lead, and solder the supply pins of each CMOS package before soldering the other pins. This enables the static protection circuitry within each CMOS device to be effective during the soldering operation. It is not necessary to solder the unused IC pins.

power socket. A look at the photograph will show a mounting bracket for a 9V battery. If battery life is more important than the frequency over which the prescaler operates, then the zener can be removed from circuit by removing the copper track between pin 15 and 16 on IC3 and replacing the 330 ohm resistor with a link. This will reduce the current drain from the battery to about 3mA. The lower operating frequency of the audio prescaler at 9V is then about 4Hz.

Incidentally, if the output voltage of the prescaler is too high to suit your frequency meter, a suitable voltage divider, with total resistance of 10k or more, may be used.