

# designideas

READERS SOLVE DESIGN PROBLEMS

## Simple fixture determines leakage of capacitors and semiconductor switches

Marián Štofka, Slovak University of Technology, Bratislava, Slovakia

The circuit in **Figure 1a** comprises a voltage follower,  $IC_1$ , and the reference-voltage source of  $IC_2$ .  $IC_1$  is an Analog Devices (www.analog.com) AD8661 op amp, which has a guaranteed input-bias current of no more than 1 pA and a typical input-bias current of 0.3 pA (**Reference 1**), and  $IC_2$  is an Analog Devices ADR391 precision voltage reference (**Reference 2**). The manufacturer trims the input offset voltage of this op amp not to exceed 100  $\mu$ V, and the typical value is 30  $\mu$ V. These properties suit this amplifier for observing

self-discharging of almost any type of capacitor. The leakage currents of solid-tantalum capacitors and those having high-quality plastic dielectrics are well above the input-bias current of voltage follower  $IC_1$ . The CUT (capacitor under test) initially charges to the reference-voltage level of 2.5V by connecting Point A to the output of  $IC_2$ . Subsequently, at some convenient time, Point A disconnects from the source of the reference voltage. A DVM (digital voltmeter) measures the output voltage of the follower at some reasonable time. The measured

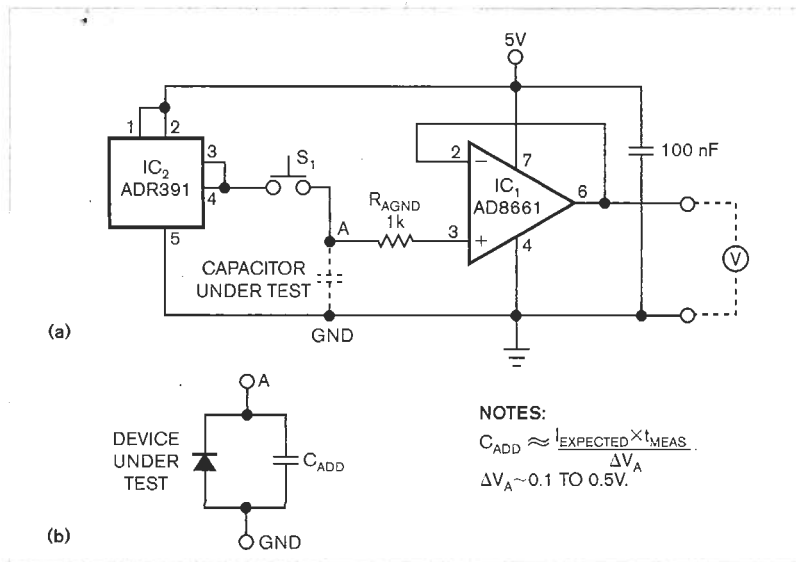


Figure 1 This simple fixture first impresses a reference voltage across a capacitor under test and then measures the voltage drop versus time at the output of the voltage follower (a). The circuit measures the leakage current of a reverse-biased active device (b).

### DIs Inside

84 Recycle precision potentiometers as useful voltage sources

88 Circuit breaker provides over-current and precise overvoltage protection

94 Paralleling decreases autozero-amplifier noise by a factor of two

94 Two transistors form high-precision, ac-mains ZCD

What are your design problems and solutions? Publish them here and receive \$150! Send your Design Ideas to [edndesignideas@reedbusiness.com](mailto:edndesignideas@reedbusiness.com).

voltage drop,  $V_O$ , with regard to initial value, should be 0.1 to 0.5V. The leakage current,  $I_O$ , is  $C \times \Delta V_O / t_{MEAS}$ , where  $C$  is the value of the CUT and  $t_{MEAS}$  is the time between releasing the connection of the CUT to the 2.5V source and the instant of readout at the voltage drop of  $V_O$ .

The fixture also allows determining leakage currents of reverse-polarized diodes and of various switching devices in the off state, such as JFETs, MOSFETs, BJTs (bipolar-junction transistors), SCRs (silicon-controlled rectifiers), and IGBTs (insulated-gate bipolar transistors). In this case, the parallel combination of the DUT (device under test) and the added capacitor,  $C_{ADD}$ , replaces the CUT (**Figure 1b**). The measurement and the formula for evaluating the value of leakage current are the same as those for leakage current in the equation  $I_O = C \times \Delta V_O / t_{MEAS}$ , but  $C_{ADD}$  substitutes for the CUT. A polystyrene-dielectric, 10-nF  $C_{ADD}$  works well for low-power devices. For high-power devices, however,

# designideas

the value of  $C_{ADD}$  should be at least 10 times the value of the parasitic capacitance of the DUT at 0V.

Further, the fixture in **Figure 1b** can also determine the values of resistors of tens of megohms to about 2 T $\Omega$ . The current in the equation  $I_o = C \times \Delta V_o / t_{MEAS}$ , in this case, is the current flowing through resistor  $R_{AGND}$  at approximately the reference voltage. The resistance is roughly:

$$R_{AGND} \approx V_{REF} \times \frac{t_{MEAS}}{C_{ADD} \times \Delta V_o},$$

or, more precisely:

$$R_{AGND} = \left( \frac{V_{REF}}{\Delta V_o} - \frac{1}{2} \right) \frac{t_{MEAS}}{C_{ADD}}.$$

In all measurements, the voltage drop of  $V_o$  should not exceed about one-fifth of the reference-voltage value to allow approximating the inherently exponential droop of  $V_o$  by a linear decrease. The pushbutton switch in **Figure 1a**,  $S_1$ , must exhibit a leakage of less than 1 pA. Stranded, isolated leads terminated with a gold-plated phosphorus-bronze pin can serve as a low-leakage switch. You can find gold-plated metal pieces in any type of high-quality connectors.

Also, you can clip the DUT or CUT between two gold-plated clips made of similar connector parts. To minimize the circuit's leakage, it uses no PCB (printed-circuit board).

## REFERENCES

- 1 AD8661 16V Low Cost, High Performance CMOS Rail-to-Rail Operational Amplifiers, [www.analog.com/en/prod/0,2877,AD8661,00.html](http://www.analog.com/en/prod/0,2877,AD8661,00.html).
- 2 ADR391 2.5V Micropower, Low Noise Precision Voltage References with Shutdown, [www.analog.com/en/prod/0,,769\\_838\\_adr391,00.html](http://www.analog.com/en/prod/0,,769_838_adr391,00.html).