

NEW IDEAS

Add-on scope multiplexer

HAVING A DUAL-TRACE SCOPE IS A LUXURY that many of us, unfortunately, must do without. However, with the simple circuit we'll describe, you can add dual-trace capability to your single-trace scope at a cost of less than \$5. Unfortunately, the device has one major "drawback," it only monitors logic levels (TTL and CMOS); but at that price, who cares!

How it works

Figure 1 shows the multiplexing circuit that lets you view two traces simultaneously. The operation of the unit revolves around three IC's: a 4093 quad NAND Schmitt-trigger, 4066 quad analog-switch, and a 7555 timer (that is used to gate IC2-b and IC2-c on or off.)

and a 7555 timer (that is used to gate IC2-b and IC2-c on or off.)

The device can be powered from a supply ranging of from 4.5 to 15 volts, and draws less than 2 mA. With a supply of 5 volts, the unit may be used to monitor TTL or CMOS logic-levels. At higher supply voltages (15 volts), it may be used to check only CMOS logic signals.

To make the operation of the unit a little easier to understand, we'll first look at the two input circuits separately and then see how the switching action of the circuit is handled.

When a high is fed to PROBE1IN, it is inverted by IC1-a and once again

by IC1-b, so that the input to IC2-a is high. That high causes the "switch contacts" in IC2-a to close. With the "contacts" closed, a high-level output is presented to the input of IC2-b.

Meanwhile, let's suppose that a high is fed to PROBE 2 IN. That signal is then inverted by IC1-d and routed to IC2-d, causing its "contacts" to open and the unit to output a logic-level high. The output of IC2-d is then fed to IC2-c.

Unless a gating pulse is presented to both IC2-c and IC2-d, *continued on page 112*

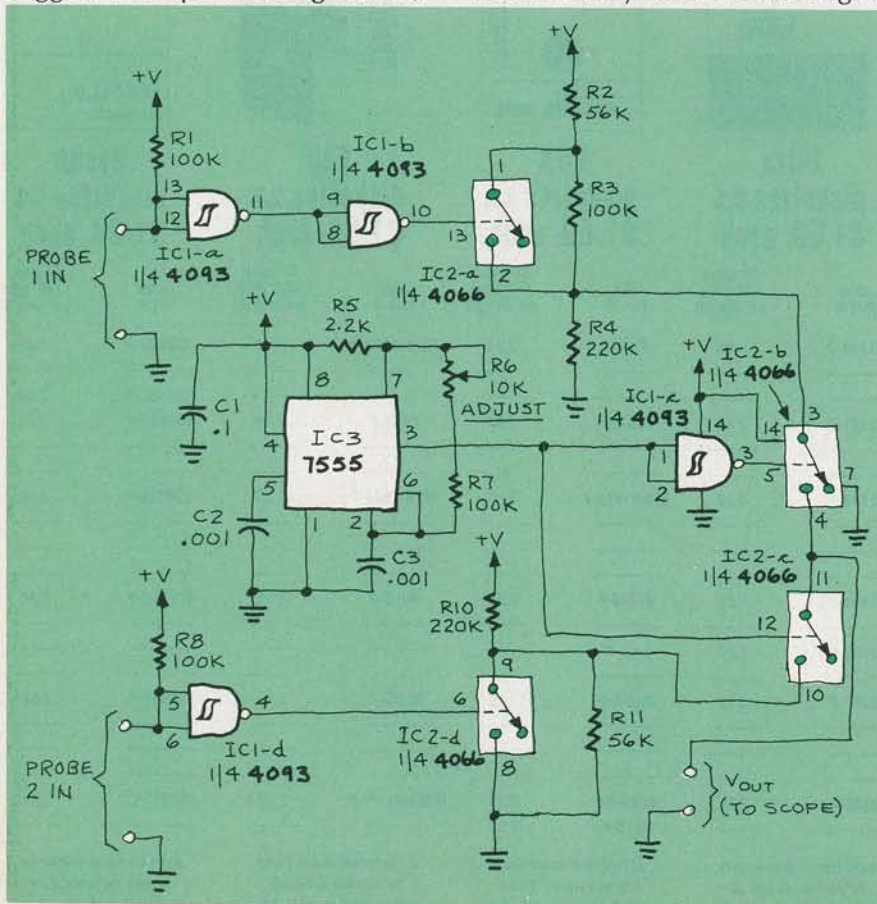


FIG.1

NEW IDEAS

This column is devoted to new ideas, circuits, device applications, construction techniques, helpful hints, etc.

All published entries, upon publication, will earn \$25. In addition, for U.S. residents only, Panavise will donate their model 333—The Rapid Assembly Circuit Board Holder, having a retail price of \$39.95. It features an eight-position rotating adjustment, indexing at 45-degree increments, and six positive lock positions in the vertical plane, giving you a full ten-inch height adjustment for comfortable working.

I agree to the above terms, and grant Radio-Electronics Magazine the right to publish my idea and to subsequently republish my idea in collections or compilations of reprints of similar articles. I declare that the attached idea is my own original material and that its publication does not violate any other copyright. I also declare that this material has not been previously published.

Title of Idea

Signature

Print Name

Date

Street

City

State

Zip

Mail your idea along with this coupon to: **New Ideas Radio-Electronics, 200 Park Ave. South, New York, NY 10003**

STATE OF SOLID STATE

continued from page 101

power-supply rejection ratio (PSRR) is 30 dB.

Figure 4 shows how the ULN-3784B is used as an amplifier with bass and treble controls.

Additional information on both devices is available on request from **Sprague Electric Company**, Semiconductor Division, 115 Northeast Cutoff, Worcester, MA 01606. Refer to Engineering Bulletin 21717.12 for the ULN-3784B and to Engineering Bulletin 21717.23 for the ULN-3705M low-voltage amplifier. **R-E**

NEW IDEAS

continued from page 32

their "contacts" will remain open and no signal will appear at the output. We use the output from pin 3 of IC3 (a 7555 timer) to gate IC2-b and IC2-c. Note that the signal from IC3 is inverted before it is fed to IC2-b but not before it is sent to IC2-c. Thus, the pulsing output from IC3 will alternately switch the display between probes

Two voltage-divider networks determine the position that the trace is to be shown on the screen. Because we want to display both signals at the same time, the high and low levels for one probe must be different from the high and low levels for the other probe. For INPUT 1, the divider is made up of resistors R2, R3, and R4, and for the other, R10 and R11.

The addition of R3 in the first voltage-divider circuit increases the voltage level of both the high-level and low-level inputs from probe 1. Thus, the probe-1 signals will be displayed at the top of the signals from probe 2. The probe-1 trace is displayed between the 3- and 4-volt mark, while the probe-2 trace is shown between zero and one-volt. That can be shown by the following formulas, which assume a high level of +5-volts.

Probe 1:

$$\text{High} \approx \frac{R_4}{R_2 + R_4} (V) \\ = \frac{220K}{56K + 220K} (5V) \approx 4V$$

$$\text{Low} \approx \frac{R_4}{R_2 + R_3 + R_4} (V) \\ = \frac{220K}{56K + 100K + 220K} (5V) \approx 3V$$

Probe 2:

$$\text{High} \approx \frac{R_{11}}{R_{10} + R_{11}} (V) \\ = \frac{56K}{220K + 56K} (5V) \approx 1V \\ \text{Low} \approx 0V$$

With the scope set to trigger on one input, signals up to 50 kHz can be monitored. That makes the circuit ideal for low to medium speed logic-level inputs. Certain frequencies can cause garbage (harmonics of the sampling frequency) to be displayed; however, adjusting potentiometer R6 will correct that.—Jeff Verive

A QUALITY TRIPLE-REGULATED POWER SUPPLY AT A LOW, LOW PRICE!!

NOT A KIT!



MODEL PS101
FULLY ASSEMBLED & TESTED!

\$ 119.88

FULL 1 YEAR REPLACE-MENT WARRANTY

— Made In The United States —

This DC triple regulated variable power supply has all the features you could ask for plus a full 1 year guarantee. Fully adjustable from 1½ VDC to 35 VDC! Three completely independent supplies that offer many advantages! They can be either a pos. supply or a neg. supply...they can also be stacked in series so that a 5V and two 15V supplies can total a 35 VDC supply or any combination of the three...(after one of the terminals is grounded to give it a reference)...for the first time you can now purchase this American made fully adjustable power supply at a price that is one-half of what you'd expect to pay!

SPECIFICATIONS

3 outputs:
Fixed 5 VDC ± 0.2V
2 variable ≤ 1½ V to ≥ 15 VDC
Polarity—floating; can be used as pos. or neg.
Ripple less than 10mV at full load,
Regulation ≤ 1% no load to full load,
Line Regulation < 0.2% 108 VAC to 135 VAC.
Current:
Fixed supply 1.0 amp max.
Variable supplies 0.5 amp max.

Protection built in, current limiting, with thermal shutdown.
Power: 108-135 VAC.
Dimensions: 8¼" x 3¼" x 7¼" (WxHxD)
Wood grain finished metal case.
Weight: 4 lbs., 9 ozs.
Lighted on/off power switch, easy-to-read Voltmeter and large binding posts.
Warranty: one year full replacement warranty from date of purchase.

DISTRIBUTOR AND REPRESENTATIVE INQUIRIES INVITED

EWE
E.W. ENGINEERING, INC.

VISA, MASTERCARD, AMEX TELEPHONE ORDERS ACCEPTED!
6 Herman Drive, E. Granby, CT 06026 □ 203/651-0285