



Constant-resistance termination

IN 1945, HENDRIK W BODE published *Network Analysis and Feedback Amplifier Design*, codifying in one classic book the filter and feedback-amplifier theory upon which much of the electronics industry still relies.

Of the many secrets his seminal work reveals, one of my favorites is the constant-resistance network (Figure 1). The figure shows only one of many forms of this circuit. As long as you scale the components such that the time constant, $Z_0 C_{IN}$, equals the time constant, L_2/Z_0 , then, in response to a step input, the rate of decrease in the admittance of the R-C leg precisely matches the rate of increase in the admittance of the L-R leg. The result is that the impedance, $Z(f)$, of the whole circuit remains constant at all frequencies. At least, it remains constant until some limit above which the parasitic aspects of the circuit take over and the C and L components no longer behave like Cs and Ls.

This circuit occasionally sees application in digital systems as a terminating network. For example, suppose C_{IN} represents the unavoidable input capacitance of

a receiver. You may then use components R_1 , R_2 , and L to complete the circuit, forming at the input a compensated termination that returns no echo regardless of the value of C_{IN} .

THE GENERAL THEORY OF CONSTANT-RESISTANCE NETWORKS BECOMES VERY IMPORTANT WHEN YOU WISH TO CONSTRUCT AN EQUALIZING FILTER AT THE END OF A LONG TRANSMISSION LINE.

In that case, the received signal, having passed through R_1 before arriving at the input terminal of the receiver, is delayed by the group delay, $\tau_{group} = R_1 C_{IN}$ of the filter thus formed. The filter's 10 to 90% rise time, $\tau_{10-90\%} = 2.2 \cdot R_1 C_{IN}$, degrades the rise time of the incoming signal. Provided these two artifacts are acceptable, the termination works in an ideal fashion.

Many other constant-resistance structures are possible. The general theory says that if you replace C_{IN} by any network a and L_2 by any network b having the impedance relationship $b = Z_0^2/a$, the input impedance of the whole structure will still equal exactly Z_0 at all frequencies. This remarkable property is provable using ordinary algebra, although the calculations are hideous and

time-consuming. One can only imagine how many long nights Bode spent in his office at Bell Labs coming up with this theory. The general theory of constant-resistance networks becomes very important when you wish to construct an equalizing filter at the end of a long transmission line. By carefully crafting impedance a , you can construct just about any arbitrary equalization function at the input terminals of the receiver. You then use impedance b to bal-

ance the network such that the input impedance of the whole structure looks like a perfect end termination.

Constant-resistance filters differ significantly from lossless L-C ladder filters, such as the popular Cauer filters you may have encountered. A lossless filter works by either passing power through the network or reflecting it back to its source. A constant-resistance filter works by either passing power through the network or shunting it off to the balancing leg of the filter, where it dissipates harmlessly in the form of heat. □

Howard Johnson, PhD, author of *High-Speed Digital Design and High-Speed Signal Propagation*, frequently conducts technical workshops for digital engineers at Oxford University and other sites worldwide. www.sigcon.com, howiej@sigcon.com.

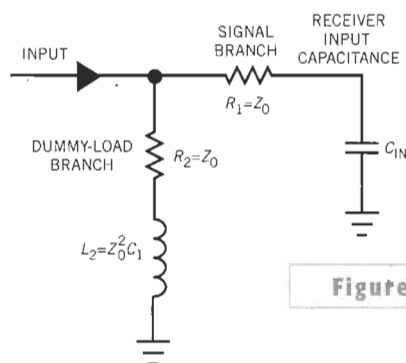


Figure 1

The input impedance of this constant-resistance network equals Z_0 at all frequencies.