Divide by three

This circuit uses only three t.t.l. i.cs to divide an input signal by three and provide an equal mark-to-space ratio output. The monostable is adjusted to produce an equal mark-to-space ratio from any input signal.

D. J. Eaton,
St. Leonards on Sea,
E. Sussex.